

Practice problems for ECE 432/532 – part 2 (HW-2) – Sp2016

For HW#2 in ECE 432/532 do 6 of the problems listed below. The more you do the more proficient you will become. A dropbox will be provided on D2L for submissions. Several areas are covered:


- a) Designing amps using unilateral devices or unilateral approximation
 - a. Amplifier design for maximum gain
 - b. Amplifier design for specific gain
- b) Working with operating and available gains
- c) Designing low-noise amplifiers

Here are some problems from Pozar (4th edition): **12.9, 12.12, 12.15, 12.16.**

The following problems are taken (some are modified) from 2nd edition of Gonzalez' book:

1. Problem 3.21: Design a microwave transistor amplifier for $G_{T,max}$ using a transistor with S parameters (50 Ohm system): $S_{11} = 0.277 \angle -59^\circ$, $S_{12} = 0.078 \angle 93^\circ$, $S_{21} = 1.94 \angle 64^\circ$, $S_{22} = 0.848 \angle -31^\circ$.

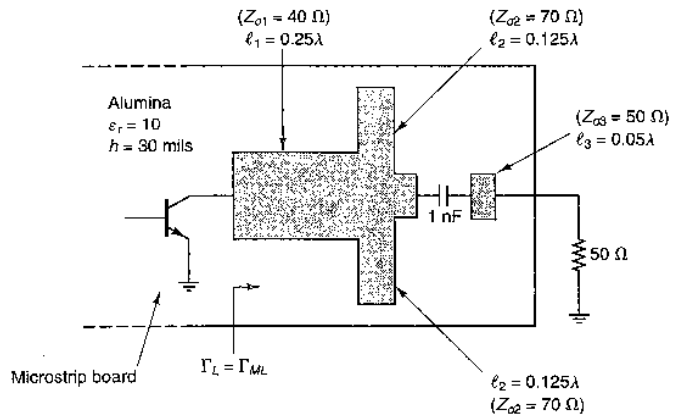
2. Prob. 3.22: The output matching network shown below was designed at 2 GHz for a simultaneous conjugate match.
 - (a) Determine Γ_{ML} .
 - (b) If the microstrip is alumina ($\epsilon_r = 10$) and $h = 30$ mils, determine the length of the 0.25λ line.



3. Prob. 3.25: Design a microwave transistor amplifier at $f = 750$ MHz to have $G_p = 10$ dB using: $S_{11} = 0.277 \angle -59^\circ$, $S_{12} = 0.078 \angle 93^\circ$, $S_{21} = 1.94 \angle 64^\circ$, $S_{22} = 0.848 \angle -31^\circ$.
4. Prob. 3.26. At 2 GHz, a GaAs FET has the following S parameters: $S_{11} = 0.7 \angle -65^\circ$, $S_{12} = 0.03 \angle 60^\circ$, $S_{21} = 3.2 \angle 110^\circ$, $S_{22} = 0.8 \angle -30^\circ$. Determine the stability and design an amplifier with $G_p = 10$ dB.
5. Prob. 4.4. The S parameters and noise parameters are: $S_{11} = 0.6 \angle -170^\circ$, $S_{12} = 0.05 \angle 16^\circ$, $S_{21} = 2 \angle 30^\circ$, $S_{22} = 0.5 \angle -95^\circ$, $F_{min} = 2.5$ dB, $\Gamma_{opt} = 0.5 \angle 145^\circ$, $R_n = 5$ Ohm. Determine:
 - a. Is the transistor unconditionally stable
 - b. What is $G_{A,max}$
 - c. Draw constant available power gain circle which is 3 dB less than $G_{A,max}$
 - d. Determine the noise figure if the transistor is used in an amplifier designed for $G_{A,max}$.


6. Prob. 4.8. Design an LNA for minimum noise figure for a transistor with $S_{11} = 0.8 \angle -51.9^\circ$, $S_{12} = 0.045 \angle 54.6^\circ$, $S_{21} = 2.15 \angle 128.3^\circ$, $S_{22} = 0.73 \angle -30.5^\circ$, $F_{\min} = 1.25$ dB, $\Gamma_{\text{opt}} = 0.73 \angle 60^\circ$, $R_n = 19.4$ Ohm.

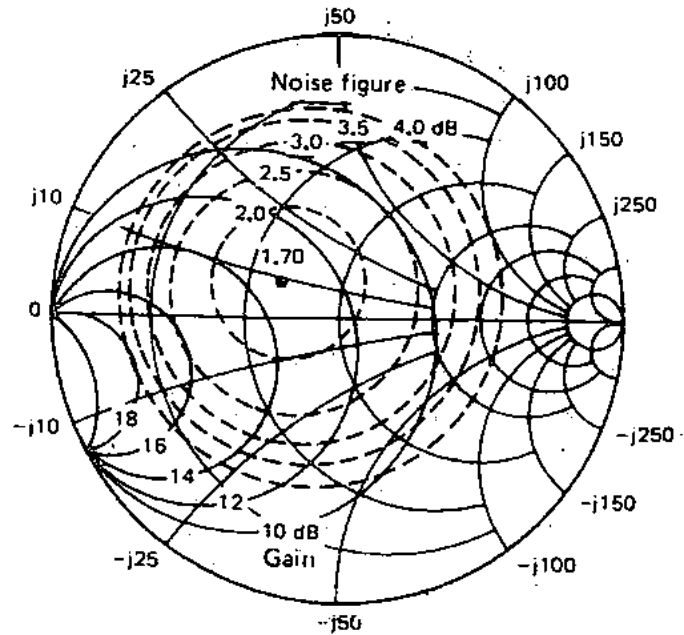7. Prob. 4.3. For the transistor with $S_{11} = 0.646 \angle -172^\circ$, $S_{12} = 0.051 \angle 13.5^\circ$, $S_{21} = 3.042 \angle 47.9^\circ$, $S_{22} = 0.642 \angle -64^\circ$: What are the noise parameters given the figure below? Find the value of Γ_s that produces an available power gain of 14 dB and a noise figure of 2 dB. Find which value of Γ_L produces $\text{VSWR}_{\text{out}} = 1$.



Frequency = 2 GHz, 10 V, 5 mA

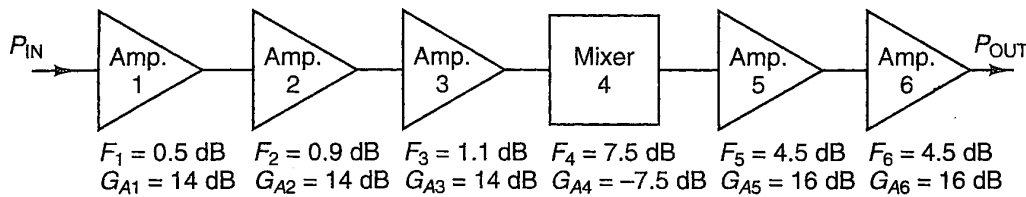8. Prob. 4.13: Consider the LNB below. Calculate the total noise figure and the available gain.



You should also be quite familiar with all the examples given in the notes. Pozar has one example of power amplifier design: example 12.9 on p. 600. For LNA design, check out his example 12.5 (unilateral design).