

Practice problems for ECE 432/532 – Sp2016


Several areas are covered:

- a) Matching problems using lumped elements and microstrip components
- b) Transistor/amplifier stability


Here are some problems from Pozar (4th edition): 12.1, 12.2, 12.3, 12.5, 12.6,

The following problems are taken (some are modified) from 2nd edition of Gonzalez' book:

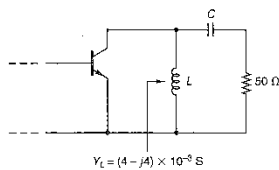
1. Prob. 2.2 a) and c).
 - a. Show that impedances having a negative real part (i.e., $z = -r + jx$) have a reflection coefficient whose magnitude is greater than 1
2. Prob. 2.11. Design the matching network in figure below that provides $Y_L = (4 - j4) \times 10^{-3} \text{ S}$ to the transistor. Find the element values at 700 MHz.



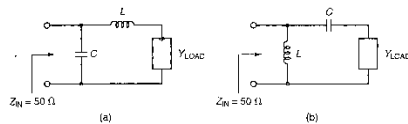3. Prob. 2.12. Two types of ELL matching networks are shown below. Select one that can match the load $Y_{LOAD} = (8 - j12) \times 10^{-3} \text{ S}$ to a 50 Ohm transmission line. Find the element values at $f = 1 \text{ GHz}$.




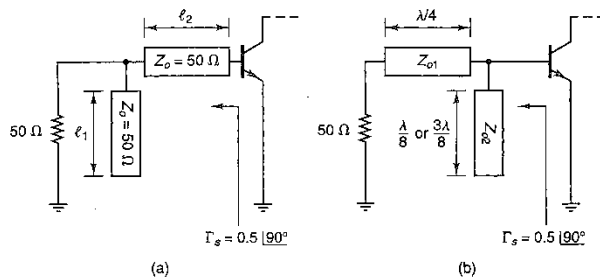4. Prob. 2.22. Design the matching networks shown below to produce the source reflection coefficient $\Gamma_s = 0.5 \angle 90^\circ$. In part b) of the figure, the appropriate length for the short-circuited stub must be selected (i.e., $\lambda/8$ or $3\lambda/8$). In addition, try to design a balanced version of the shunt stubs. (Warning: figure b) that has $\lambda/4$ line in it is a little bit different than the "usual" matching circuits we used. However, you should be able to figure out how to do this on your own).




5. Prob. 3.3. A microwave amplifier diagram is shown below. Determine G_T , G_A , and G_p if $\Gamma_s = 0.49 \angle -150^\circ$, $\Gamma_L = 0.56 \angle 90^\circ$, and the S parameters of the transistor are: $S_{11} = 0.54 \angle 165^\circ$, $S_{12} = 0.09 \angle 20^\circ$, $S_{21} = 2 \angle 30^\circ$, $S_{22} = 0.5 \angle -80^\circ$. Calculate P_{AVS} , P_{IN} , P_{AVN} , and P_L if source voltage $E_1 = 10 \angle 30^\circ$, source impedance $Z_1 = 50 \text{ Ohm}$ and load impedance $Z_2 = 50 \text{ Ohm}$.

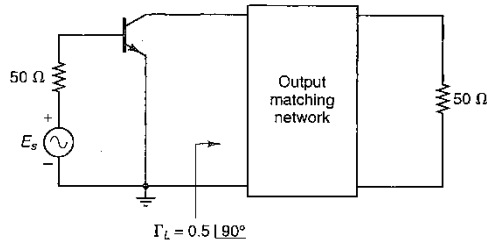6. Prob. 3.4: The S parameters of transistor are: $S_{11} = 0.7 \angle 30^\circ$, $S_{12} = 0$, $S_{21} = 4 \angle 90^\circ$, $S_{22} = 0.5 \angle 0^\circ$. Amplifier is shown in figure below where output matching network produces $\Gamma_L = 0.5 \angle 90^\circ$. Determine the values of G_T , G_p



and G_A .

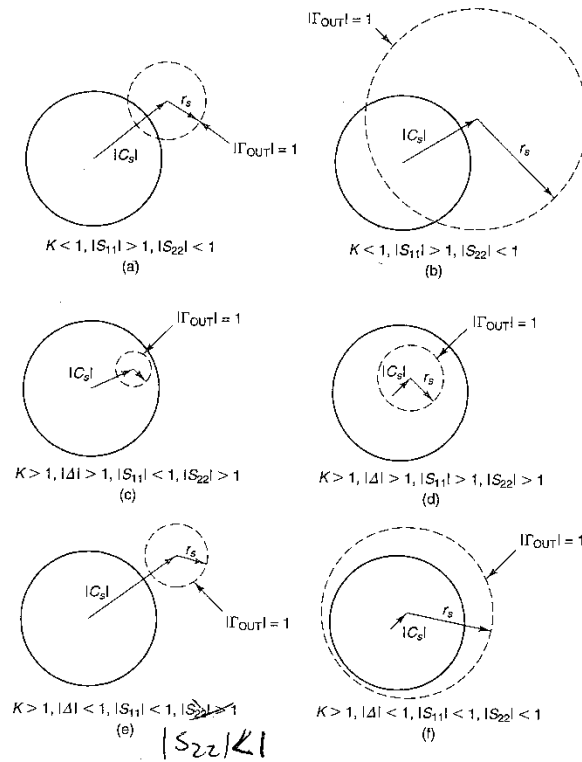7. Prob. 3.5. In each of the stability circles shown below indicate clearly the possible locations for stable Γ_S (source



reflection coeff.)

8. Prob. 3.7.: The scattering parameters for three different transistors are given below. Determine the stability in each case and in a potentially unstable case, draw the input and output stability circles.
- $S_{11} = 0.674 \angle -152^\circ$, $S_{12} = 0.075 \angle 6.2^\circ$, $S_{21} = 1.74 \angle 36.4^\circ$, $S_{22} = 0.6 \angle -92.6^\circ$
 - $S_{11} = 0.385 \angle -55^\circ$, $S_{12} = 0.045 \angle 90^\circ$, $S_{21} = 2.7 \angle 78^\circ$, $S_{22} = 0.89 \angle -26.5^\circ$
 - $S_{11} = 0.7 \angle -50^\circ$, $S_{12} = 0.27 \angle 75^\circ$, $S_{21} = 5 \angle 120^\circ$, $S_{22} = 0.6 \angle 80^\circ$
9. Prob. 3.14: Show how resistive loading can stabilize a transistor whose S parameters at $f=750$ MHz are: $S_{11} = 0.69 \angle -78^\circ$, $S_{12} = 0.033 \angle 41.4^\circ$, $S_{21} = 5.67 \angle 123^\circ$, $S_{22} = 0.84 \angle -25^\circ$.

You should also be quite familiar with all the examples given in the notes. For LNA design, check out his example 12.5 (unilateral design).